

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 1, 2016/2017

EMG4076 – ELECTROMAGNETIC INTERFERENCE (TE, RE)

21 OCTOBER 2016
9.00 A.M. – 11.00 A.M.
(2 Hours)

INSTRUCTION TO STUDENT

1. This Question paper consists of 5 pages including cover page with 4 Questions only.
2. Attempt all **FOUR** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please write all your answers in the answer Booklet provided.

Question 1

- (a) Consider three parallel wires, two are signal leads (lead-1 and lead-2) and the third is a common signal-return lead (lead-G). The circuit of Figure Q1 represents the inductive coupling between the circuits.

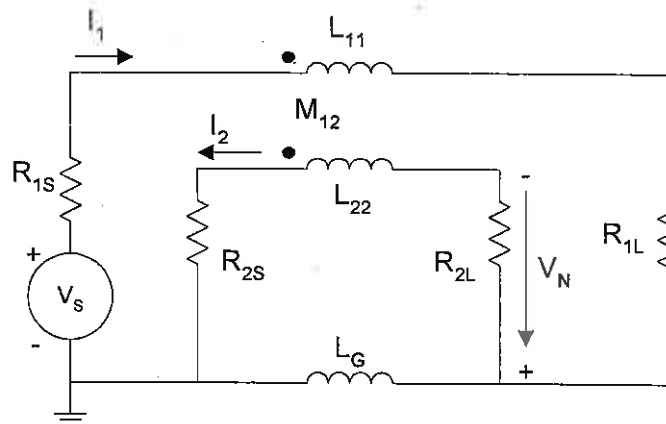


Figure Q1

- (i) Show that the noise voltage V_N can be expressed as

$$V_N = K \frac{j\omega}{(j\omega + s_a)(j\omega + s_b)} V_s$$

where K , s_a and s_b are unknowns to be determined.

[12 marks]

- (ii) Derive an approximate expression for V_N at low frequency, mid-frequency and high frequency.

[6 marks]

- (iii) Draw the equivalent circuit if lead-1 is shielded in order to reduce magnetic coupling.

[4 marks]

- (b) Suggest three (3) techniques that can be applied to reduce capacitive coupling between conductors.

[3 marks]

Continued...

Question 2

- (a) With the aid of diagrams, briefly explain the differences between 'multipoint ground' and 'hybrid ground.'

[10 marks]

- (b) Layout design requires knowledge of how each current flows and returns to its source.


- (i) Explain how micro strip can reduce the electromagnetic interference (EMI) for a double layer printed circuit board (PCB).

[5 marks]

- (ii) State an alternative way to reduce EMI for a single layer PCB.

[2 marks]

- (c) Consider a signal source that is connected to the load resistor using a pair of wires as in **Figure Q2**. The mutual inductance (M) between the two wires increases when they are placed closer together. A common ground-wire exists in the electronic system.

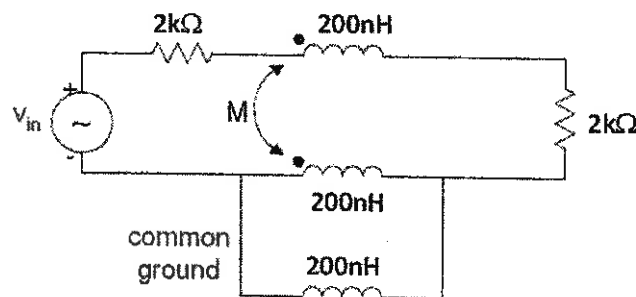**Figure Q2**

- (i) Calculate the percentage of return current diverted through the common ground for values of mutual inductance, $M=190$ nH, $M=100$ nH and $M=0$.

[6 marks]

- (ii) From your answer in (i), briefly explain which value of mutual inductance, M that will greatly reduce the electromagnetic interference in the circuit.

[2 marks]

Continued...

Question 3

- (a) Sketch the graph of wave impedance Z_w versus electrical length ($0.01\lambda - 10\lambda$) for electric and magnetic sources.

[6 marks]

- (b) Consider two 1-meter parallel wires separated at 0.5mm carrying equal and opposite current of 200mA at 100MHz. An antenna (oriented parallel to the wire) is used to measure the radiated emission at a distance 3m away from the wires. If the antenna factor is 20dB,

- (i) Determine whether the receiver antenna is in the near-field or far-field region.

[2 marks]

- (ii) Assuming negligible loss for the cable connecting the antenna to the spectrum analyzer, determine the voltage measured by a spectrum analyzer in dB μ V.

[5 marks]

$$[\text{Hint: } E_{loop} = \eta \frac{k^2 I_d A}{4\pi r}]$$

- (c) A panel, 12 cm wide and 36 cm high, is attached to a cabinet by 24 equally spaced screws around its perimeter, including one screw at each corner. The equipment in the cabinet generates a 150 MHz signal. Assume all the phases of the signals from all slots are equal and neglect any interference to aperture currents from adjacent slots,

- (i) Calculate the attenuation of this signal when it passes through the resulting slots and reach the receiving antenna 30 m away from the shield.

[5 marks]

[Hint: Attenuation A due to a slot of length l at a distance r from the slot is approximately $A = 73 - 132.45 \frac{l}{\lambda} + 20 \log \frac{r}{\lambda}$ dB where λ is the wavelength of the signal.

- (ii) If 8 equally spaced screws are used, including one at each corner, how much is the attenuation when the signal pass through the resulting slots to reach the receiving antenna in (c)(i)?

[4 marks]

- (iii) From your answer in (c)(i) and (c)(ii), which case is more effective in reducing the electromagnetic interference (EMI). Explain your answer.

[3 marks]

Continued...

Question 4

- (a) Explain the term electromagnetic compatibility (EMC) and state one of the EMC standards bodies for each of the following: International, European and United States.

[2+3 marks]

- (b) An antenna is connected to a spectrum analyzer using a 10 meters coaxial cable to measure the radiated emission from equipment under test (EUT). The distance between the EUT and the antenna is 3 meters. At 200MHz, the loss of the coaxial cable is 1.5 dB per meter and the antenna factor is 4dB. If the reading on the spectrum analyzer is 20dB μ V,

- (i) Compute the electric field strength at the antenna in dB μ V/m.

[3 marks]

- (ii) The EN55022 radiated emission limits are given in **Table Q4**. Compute the Class B limits in dB μ V/m at 3 meter distance.

[4 marks]

Table Q4

Frequency Range (MHz)	Class A Limit at 10m (μ V/m)	Class B Limit at 10m (μ V/m)
30 to 230	100	32
230 to 1000	224	71

- (iii) Evaluate whether the product pass or fail the EN55022 Class B radiated emission test.

[2 marks]

- (c) Sketch the setup of an automated system for radiated emission measurements. Describe the measurement procedure.

[11 marks]

End of Page